

# Battery Circuit



Aim: to make the globe light up.

You will need: a battery holder, two batteries, a globe, a globe holder

What to do:

Put the batteries in the battery holder.

Screw the globe into the globe holder.

Thread the wires into the holes in the metal at the bottom of the globe holder.

Have you achieved your aim? Yes, if your globe lights up.